will keep FAST FORWARD in mind and we would appreciate any support that you could give us in the line of news, available munications field. It would also help us immensely if you films or videotapes and people we might contact in the comwould like to contact us. could In thanking you for your help on our past season, we hope you pass along our name and address to anyone you may feel

Thanks again, and we hope to hear from you soon.

For the FAST FORWARD crew,



FAST FORWARD Producer (416) 484-2637

Building an S-100 Power Supply

from Off-the-Shelf Components

outputs of +8 volts @15 amps, +16 volts @ 3 amps, and -16 volts @ 3 amps. A similar approach could, of course, be used The circuit uses full-wave voltage tripling to obtain nominal S-100 power supply designed around a single off-the-shelf unless it is absolutely necessary. are expensive; one is not inclined to use two or more of them voltage power supply is that most off-the-shelf transformers One of the problems usually encountered in building a multipletransformer and a bevy of surplus electrolytic capacitors. provide only one or two output voltages. for other voltages and/or currents. This article describes an Since transformers

of +16 volts with respect to ground. The -16 volt output is obtained by using a voltage tripler (D1, D2, D5, D6, D7, D8, C1, C2, C4, C5, C6) to give -24 volts with respect to the centre-tap, or -16 volts with respect to ground. delivers +8 volts with respect to the centre-tap, for a total of Cl and C2 are grounded. A second full-wave centre-tapped rectifier circuit of the opposite polarity (D3, D4, C3) the +8-volt output instead of the common. tapped rectifier configuration (D1, D2, C1, C2) with a slight twist: the polarities are such that the centre-tap becomes The heart of the circuit is a conventional full-wave centre-The -16 volt output is The negative side

Bridge rectifiers (2 of them) could be used in place of the

who learned the hard way.) above 7.5 volts under load. half a volt each, Shottky diodes are needed to keep the output Since the ripple and secondary losses at full load are about output. eight diodes, but Shottky diodes provide an extra half volt of tage spikes, and their price - about \$7.00 a crack! approximately 8.1 volts peak output with ordinary diodes. fast switching, their vulnerability to damage by reverse vol-(R1, C7) is mandatory with Shottky diodes because of their The transformer is rated 12.6 VCT RMS, which gives Note that transient protection (Guess

by Gifford Toole

120 VAC Cic GND

Parts List

33 uF 50 V

D1, D2 D3-D8 R1 25 A 20 V Shottky diodes (TRW SD41, Motorola MBR2520) 3 A 50 V diodes (1N5400 or equivalent)

330 ohm 0.5 watt resistor 2.6 VCT 20 A RMS transformer (Hammond 167V12)

Text Editors

by Ross Cooling

able to easily it's in memory.
it from a simpl inputting ASCII information into the computers memory and is A text editor a simple monitor command to input ASCII information. make modifications S It is this latter part that truly seperates Ωı software program to the that information once